

Cambridge Technicals Engineering

Unit 4: Principles of electrical and electronic engineering

Level 3 Cambridge Technical Certificate/Diploma in Engineering
05822 - 05825 & 05873

Mark Scheme for June 2023

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

© OCR 2023

MARKING INSTRUCTIONS

PREPARATION FOR MARKING

RM ASSESSOR

1. Make sure that you have accessed and completed the relevant training packages for on-screen marking: *RM Assessor Assessor Online Training*; *OCR Essential Guide to Marking*.
2. Make sure that you have read and understood the mark scheme and the question paper for this unit. These are posted on the RM Cambridge Assessment Support Portal <http://www.rm.com/support/ca>
3. Log-in to RM Assessor and mark the **required number** of practice responses (“scripts”) and the **number of required** standardisation responses.

YOU MUST MARK 5 PRACTICE AND 10 STANDARDISATION RESPONSES BEFORE YOU CAN BE APPROVED TO MARK LIVE SCRIPTS.

MARKING

1. Mark strictly to the mark scheme.
2. Marks awarded must relate directly to the marking criteria.
3. The schedule of dates is very important. It is essential that you meet the RM Assessor 50% and 100% deadlines. If you experience problems, you must contact your Team Leader (Supervisor) without delay.
4. If you are in any doubt about applying the mark scheme, consult your Team Leader by telephone or by email.
5. **Crossed Out Responses**
Where a candidate has crossed out a response and provided a clear alternative then the crossed out response is not marked. Where no alternative response has been provided, examiners may give candidates the benefit of the doubt and mark the crossed out response where legible.

Multiple Choice Question Responses

When a multiple choice question has only a single, correct response and a candidate provides two responses (even if one of these responses is correct), then no mark should be awarded (as it is not possible to determine which was the first response selected by the candidate).

When a question requires candidates to select more than one option/multiple options, then local marking arrangements need to ensure consistency of approach.

Contradictory Responses

When a candidate provides contradictory responses, then no mark should be awarded, even if one of the answers is correct.

Short Answer Questions (requiring only a list by way of a response, usually worth only **one mark per response**)

Where candidates are required to provide a set number of short answer responses then only the set number of responses should be marked. The response space should be marked from left to right on each line and then line by line until the required number of responses have been considered. The remaining responses should not then be marked. Examiners will have to apply judgement as to whether a 'second response' on a line is a development of the 'first response', rather than a separate, discrete response. (The underlying assumption is that the candidate is attempting to hedge their bets and therefore getting undue benefit rather than engaging with the question and giving the most relevant/correct responses.)

Short Answer Questions (requiring a more developed response, worth **two or more marks**)

If the candidates are required to provide a description of, say, three items or factors and four items or factors are provided, then mark on a similar basis – that is downwards (as it is unlikely in this situation that a candidate will provide more than one response in each section of the response space.)








Longer Answer Questions (requiring a developed response)

Where candidates have provided two (or more) responses to a medium or high tariff question which only required a single (developed) response and not crossed out the first response, then only the first response should be marked. Examiners will need to apply professional judgement as to whether the second (or a subsequent) response is a 'new start' or simply a poorly expressed continuation of the first response.

6. Always check the pages (and additional lined pages if present) at the end of the response in case any answers have been continued there. If the candidate has continued an answer there then add an annotation to confirm that the work has been seen.
7. There is a NR (No Response) option. Award NR (No Response)
 - if there is nothing written at all in the answer space
 - OR if there is a comment which does not in anyway relate to the question (e.g. 'can't do', 'don't know')
 - OR if there is a mark (e.g. a dash, a question mark) which isn't an attempt at the questionNote: Award 0 marks - for an attempt that earns no credit (including copying out the question)

8. The RM Assessor **comments box** is used by your team leader to explain the marking of the practice responses. Please refer to these comments when checking your practice responses. **Do not use the comments box for any other reason.** If you have any questions or comments for your team leader, use the phone, the RM Assessor messaging system, or e-mail.
9. Assistant Examiners will email a brief report on the performance of candidates to your Team Leader (Supervisor) by the end of the marking period. Your report should contain notes on particular strength displayed as well as common errors or weaknesses. Constructive criticism of the question paper/mark scheme is also appreciated.

10. Annotations

Annotation	Meaning
	Correct response worthy of a mark. Number of ticks = number of marks awarded.
	Incorrect response
	Missing something/incomplete response
	Error carried forward
	Benefit of doubt
	No benefit of the doubt
	Rounding error


Mark scheme abbreviations:

Wtte: words to that effect


Ecf: error carried forward


11. Subject-specific marking instructions

- In all numerical calculation questions a correct response will gain all marks unless specified otherwise.
- Rounding of answers should be to the same number of significant figures as the data in the question, or, otherwise, an answer will be correct provided it rounds to the correct answer.
- Symbols used in circuit diagrams must identify relevant components uniquely and unambiguously.


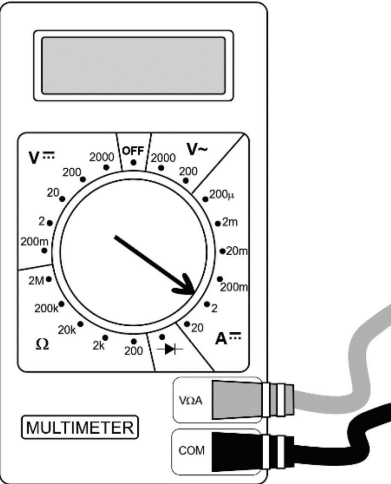
Question		Answer	Marks	Guidance
1	(a)	 <p>Arrow pointing to 2 A dc</p>	1	Synoptic mark from unit 2: LO 1.1
1	(b)	(i) <p>$P = 0.6 \text{ W}$ $t = 5 \text{ mins} = 5 \times 60 \text{ s} = 300 \text{ s}$ $W = Pt = 0.6 \times 300 = \mathbf{180} \text{ (J)}$</p>	1 1	Correctly converts to minutes to seconds [1] Synoptic mark from unit 2: LO 1.1 Correctly multiplies power by time [1] ECF from seconds conversion Award 1 mark only for an answer of 3J (not converting time to seconds)
1	(b)	(ii) <p>$V = 6 \text{ V}$ $P_1 = 0.6 \text{ W}$ $I_1 = \frac{P_1}{V} = \frac{0.6}{6} = \mathbf{0.1} \text{ (A)}$</p>	1	


Question			Answer	Marks	Guidance
1	(b)	(iii)	$R_1 = \frac{V}{I_1} = \frac{6}{0.1} = 60 \text{ } (\Omega)$ <p>OR</p> $R_1 = \frac{V^2}{P_1} = \frac{6^2}{0.6} = 60 \text{ } (\Omega)$	1	Allow ecf for I_1 from 1(b)(ii)
1	(c)		$I = 500 \text{ mA} = 0.5 \text{ A}$ $I_2 = I - I_1 = 0.5 - 0.1 = 0.4 \text{ A}$ $R_2 = \frac{V}{I_2} = \frac{6}{0.4} = 15 \text{ } (\Omega)$	1 1	Correctly calculates current through L_2 [1] allow ecf (mark for application of Kirchoff's 1 st law)
1	(d)		$P_2 = I_2 V = 0.4 \times 6 = 2.4 \text{ (W)}$ <p>OR</p> $P_2 = I_2^2 R_2 = 0.4^2 \times 15 = 2.4 \text{ (W)}$ <p>OR</p> $P_2 = V_2^2 / R_2 = 6^2 / 15 = 2.4 \text{ (W)}$	1	Or any other valid method [1] Allow ecf from 1c for R_2 and I_2

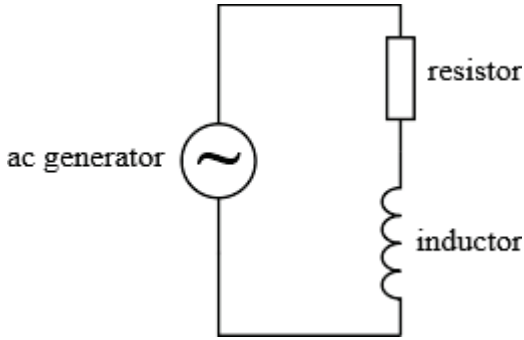
Question		Answer	Marks	Guidance	
2	(a)	Direction of current flow changes Periodically with time. e.g. Current changes direction periodically OR Current keeps changing direction	1 1	Do not accept 'flows in both directions' or 'flows both ways'.	
2	(b)	Correct symbols for inductor and resistor Correct symbol for AC supply, all three components labelled and in series  <p>The diagram shows a rectangular circuit loop. On the left vertical wire, there is a circle containing a tilde symbol (~), labeled 'ac generator'. On the right vertical wire, there is a rectangle labeled 'resistor' above a coil labeled 'inductor'. The top and bottom horizontal wires are solid lines.</p>	1 1		
2	(c)	(i)	40 (V)	1	
2	(c)	(ii)	500 (μs)	1	

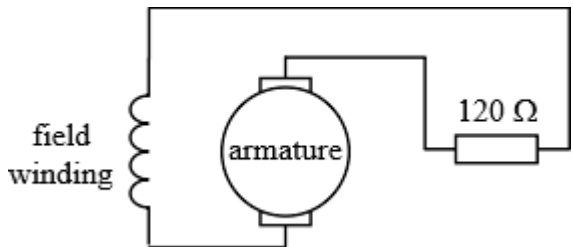Question			Answer	Marks	Guidance
2	(c)	(iii)	$T = 500 \mu\text{s} = 5 \times 10^{-4} \text{ s}$ $f = 1/T = 1/5 \times 10^{-4} = \mathbf{2000} \text{ (Hz)}$	1 1	Synoptic mark from unit 2: LO 1.1 Ecf on unit conversion/their T from 2cii Accept $f = 2 \text{ kHz}$ with prefix added to unit (or $f = 0.002 \text{ MHz}$) Correct answer 2 marks
2	(c)	(iv)	$\Delta t = 125 \mu\text{s} [\pm 10 \mu\text{s}] \text{ OR } 375 \mu\text{s} [\pm 10 \mu\text{s}]$ $\phi = 360^\circ \times \Delta t/T = 360 \times 125/500 = \pm 90^\circ [\pm 7^\circ] \text{ OR } \pm 270^\circ [\pm 7^\circ]$	1 1	Evidence of finding time difference (including as proportion of period). Converting time (or fraction of period) to angle. Correct answer by any other method [2]
2	(c)	(v)	$\phi \times 2\pi/360 = 90 \times 2\pi/360 = \pi/2 \text{ rad} = 1.57 \text{ rad} [\pm 0.13 \text{ rad}]$ OR $\phi \times 2\pi/360 = 270 \times 2\pi/360 = 3\pi/2 \text{ rad} = 4.71 \text{ rad} [\pm 0.13 \text{ rad}]$	1	Accept $\pi/2 \text{ rad}$ or $1/2\pi \text{ rad}$ Accept their 2civ converted to radians Synoptic mark from unit 1: LO 4.1
3	(a)		Labelled armature and field winding providing power to 120Ω resistor Armature and field winding connected in series with 120Ω resistor e.g. <div style="text-align: center;">  <p>The diagram shows a series circuit. On the left is a coil labeled 'field winding'. To its right is a circle labeled 'armature'. Further right is a rectangular component labeled '120 Ω'. All three components are connected in a single loop by wires.</p> </div>	1 1	Accept unlabelled armature/field winding where symbols are clearly drawn Any arrangement that puts all parts in series regardless of order Allow additional series resistor

Question			Answer	Marks	Guidance
3	(b)	(i)	$I = \frac{V}{R} = \frac{8.2}{120} = \mathbf{0.068 (A)}$	1	Synoptic mark from unit 2: LO 3.6
3	(b)	(ii)	$V = E - I_a R_t$ where $R_t = R_a + R_f$ $E = V + I(R_a + R_f) = 8.2 + 0.068(\mathbf{25 + 18})$ $= \mathbf{11.14}$ V	1 1 1	Evidence of selecting the correct equations Correct value (ecf from 3bi) Correct units Synoptic mark from unit 2: LO 1.1
3	(c)	(i)	A motor converts electrical energy to kinetic (or mechanical) energy/motion (wtte) A generator converts kinetic (or mechanical) energy/motion to electrical energy/electricity (wtte)	1 1	
3	(c)	(ii)	$V = E + I_a R_t$ where $R_t = R_a + R_f$ $I_a = \frac{V - E}{R_a + R_f} = \frac{24 - 17}{25 + 18}$ $= \mathbf{0.16 (A)}$	1 1	Evidence of selecting the correct equations Correct answer
3	(c)	(iii)	Shunt-wound (self-excited) DC motor Any one of: <ul style="list-style-type: none"> Because the speed of a shunt-wound motor is not strongly dependent on load (wtte) Because the speed of a series-wound motor is much higher when the load is reduced (wtte) 	1 1	Accept suitable motors not on specification with valid explanations (e.g. permanent magnet dc motor, brushless dc motor, separately excited dc motor) for 2 marks

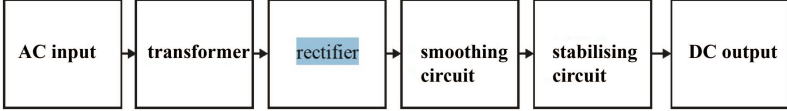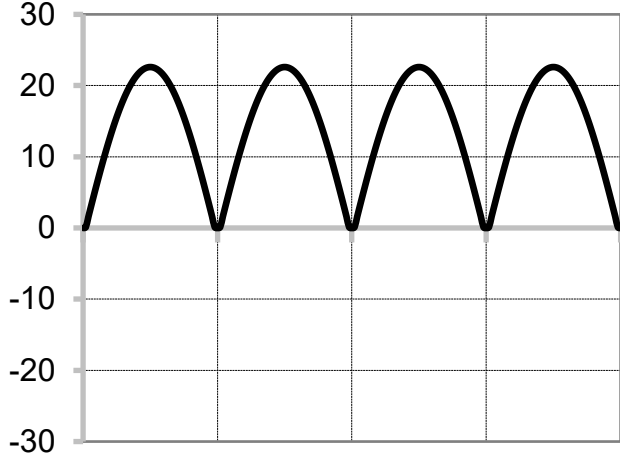Question		Answer	Marks	Guidance
4	(a)		5	1 mark for each correctly placed label in blocks 1 and 2 and 3,4 and 5 Block 3 rectifier is given in the question
4	(b)	Convert AC to DC (wtte)	1	
4	(c) (i)	... input is 24 V, B and D diodes input is 0 V, no diodes input is -24 V, A and C diodes ...	1 1 1	Accept 0
4	(c) (ii)	All positive Full wave rectified, same period 	1 1	Regardless of polarity

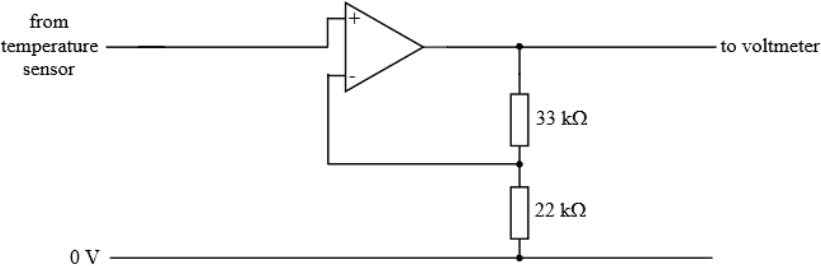Question			Answer	Marks	Guidance
5	(a)	(i)	voltage gain = $\frac{V_{out}}{V_{in}} = \frac{5.5}{2.2} = 2.5$	1	
5	(a)	(ii)	Resistor from output to – Resistor from – to 0 V Temperature sensor to + Output to voltmeter e.g.  Using Gain = $1 + R_f / R_2$, ratio $R_f : R_2 = 3 : 2$	1 1 1 1	Disregard any resistor from temperature sensor to 0 V or + input Accept any values for resistors in the correct ratio. ECF from 5(a)(i) for gain.
5	(b)		[very] high input impedance/resistance (wtte)	1	Accept infinite input impedance

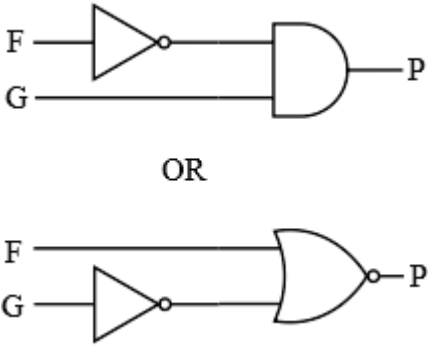Question	Answer	Marks	Guidance
5 (c)	<p>-5.9 V Evidence of adding two voltages together (5.5 V + 6.3 V) Answer of correct magnitude 5.9 Negative value –</p> $V_{out} = -\frac{R_f}{R_{in}}(V_1 + V_2)$ $= -\frac{15000}{30000} \times (5.5 + 6.3)$ $= -5.9 \text{ (V)}$	<p>1 1 1</p>	
6 (a)	<p>Can have only one of two possible values High or low voltage Binary signals 0 or 1</p>	<p>1</p>	
6 (b)	<p>One input inverted, one input not inverted into 2-input logic gate Correct logic function</p>  <p style="text-align: center;">OR</p>	<p>1 1</p>	<p>Accept any circuit that achieves the function regardless of complexity</p>
6 (c) (i)	<p>EOR / XOR / ExOR / Exclusive-OR</p>	<p>1</p>	
6 (c) (ii)	<p>$R = J \oplus K$</p>	<p>1</p>	

Question			Answer	Marks	Guidance																																													
6	(c)	(iii)	All possible combinations of J, K and L	1	If not all possible combinations of input given allow max 1 mark for 4 fully correct rows																																													
			Column R correct	1																																														
			Column S correct	1																																														
			<table border="1"> <thead> <tr> <th>J</th> <th>K</th> <th>L</th> <th>R</th> <th>S</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	J		K	L	R	S	0	0	0	0	0	0	0	1	0	1	0	1	0	1	1	0	1	1	1	0	1	0	0	1	1	1	0	1	1	0	1	1	0	0	0	1	1	1	0	1	
			J	K		L	R	S																																										
			0	0		0	0	0																																										
			0	0		1	0	1																																										
			0	1		0	1	1																																										
			0	1		1	1	0																																										
			1	0		0	1	1																																										
1	0	1	1	0																																														
1	1	0	0	0																																														
1	1	1	0	1																																														

Need to get in touch?

If you ever have any questions about OCR qualifications or services (including administration, logistics and teaching) please feel free to get in touch with our customer support centre.

Call us on

01223 553998

Alternatively, you can email us on

support@ocr.org.uk

For more information visit

 ocr.org.uk/qualifications/resource-finder

 ocr.org.uk

 [Twitter/ocrexams](https://twitter.com/ocrexams)

 [/ocrexams](https://twitter.com/ocrexams)

 [/company/ocr](https://www.linkedin.com/company/ocr)

 [/ocrexams](https://www.youtube.com/ocrexams)



CAMBRIDGE
UNIVERSITY PRESS & ASSESSMENT

OCR is part of Cambridge University Press & Assessment, a department of the University of Cambridge.

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored. © OCR 2023 Oxford Cambridge and RSA Examinations is a Company Limited by Guarantee. Registered in England. Registered office The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA.

Registered company number 3484466. OCR is an exempt charity.

OCR operates academic and vocational qualifications regulated by Ofqual, Qualifications Wales and CCEA as listed in their qualifications registers including A Levels, GCSEs, Cambridge Technicals and Cambridge Nationals.

OCR provides resources to help you deliver our qualifications. These resources do not represent any particular teaching method we expect you to use. We update our resources regularly and aim to make sure content is accurate but please check the OCR website so that you have the most up-to-date version. OCR cannot be held responsible for any errors or omissions in these resources.

Though we make every effort to check our resources, there may be contradictions between published support and the specification, so it is important that you always use information in the latest specification. We indicate any specification changes within the document itself, change the version number and provide a summary of the changes. If you do notice a discrepancy between the specification and a resource, please [contact us](#).

Whether you already offer OCR qualifications, are new to OCR or are thinking about switching, you can request more information using our [Expression of Interest form](#).

Please [get in touch](#) if you want to discuss the accessibility of resources we offer to support you in delivering our qualifications.